


University of Southern California

Viterbi School of Engineering


MOS Logic Design Basics

Combinational Logic

 - A combinational logic cell, logic circuit or gate is generally a multiple input, single output system that performs a Boolean function
- In the positive logic convention, logic 1 is shown by high voltage V_{DD} and logic 0 by low voltage of zero





 - Transistors can be thought as a switch controlled by its gate signal
- NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1

  
- PMOS switch closes when switch control input is low



PMOS Transistors pass a “strong” 1 but a “weak” 0

Threshold Drops

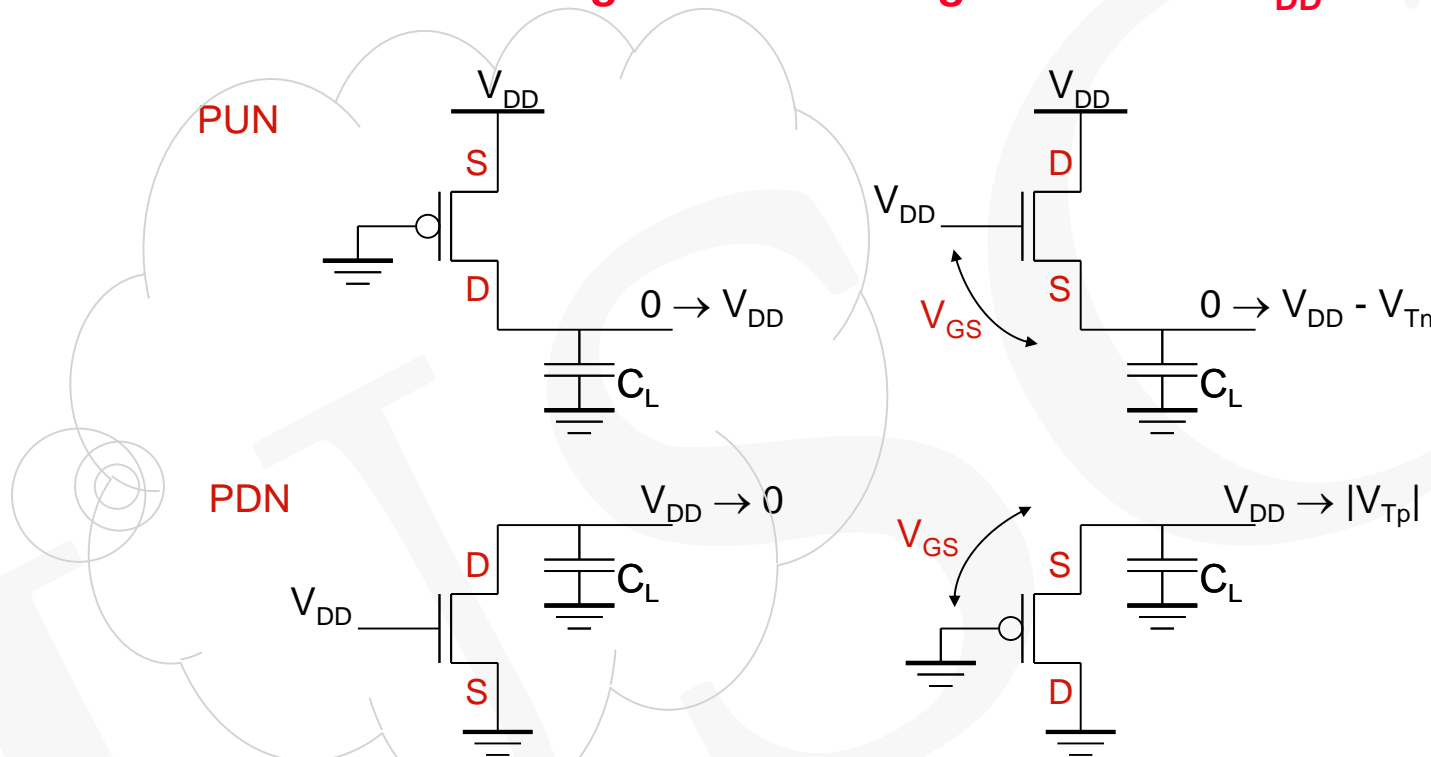
- **NMOS:** A device which is good in shorting its drain to the ground
- **PMOS:** A device which is good in shorting its drain to V_{DD}



- **NMOS** passes a strong zero and a weak one
- **PMOS** passes a strong one and a weak zero
- **Note:** NMOS gate = 0, PMOS gate = 1 are in high Impedance


CMOS Transmission Gates (Pass Gates)

 - The **CMOS transmission gate (TG)** consists of one NMOS and one PMOS transistor, connected in parallel
- The **CMOS TG** operates as a bidirectional switch between nodes A and B, which is controlled by signal C




Four different representations of the CMOS transmission gate


CMOS Transmission Gates – Examples

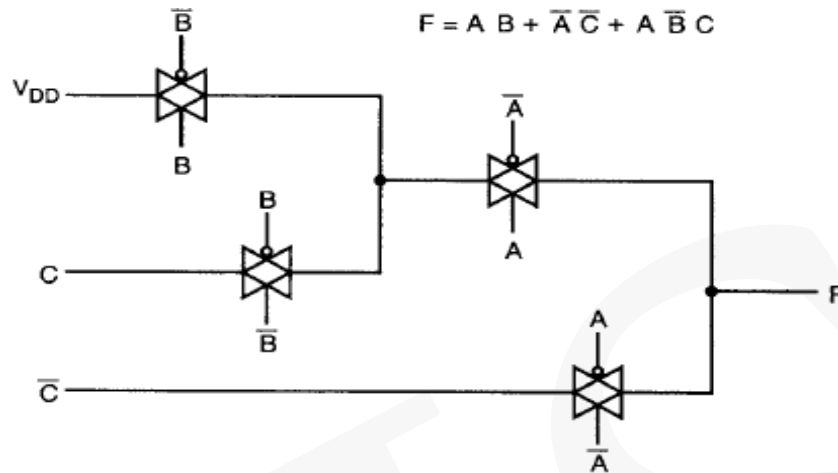

Two-Input Multiplexer

 



Complementary MOS (CMOS)

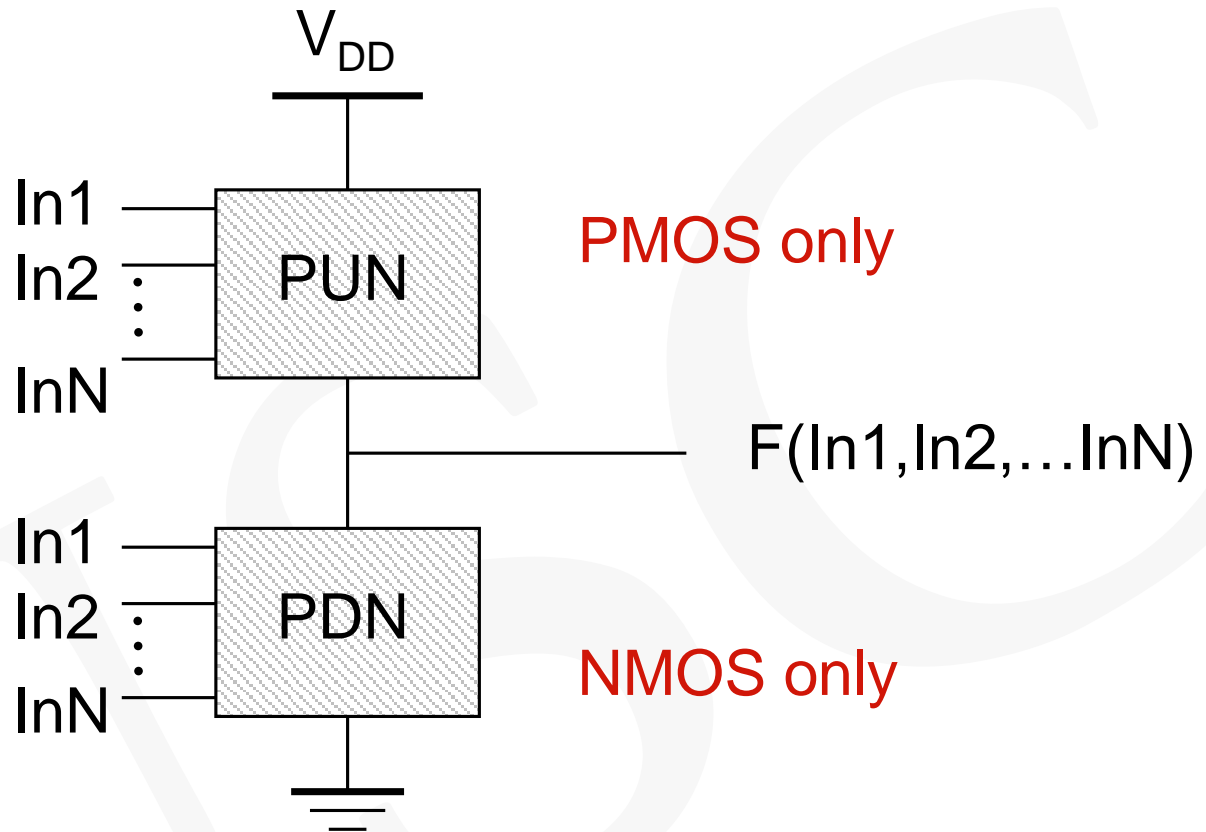


- PUN and PDN are dual Logic Networks

Pull-up and Pull-down Networks

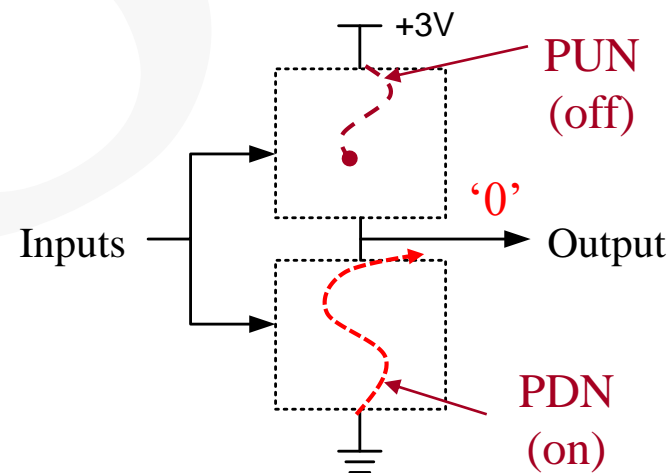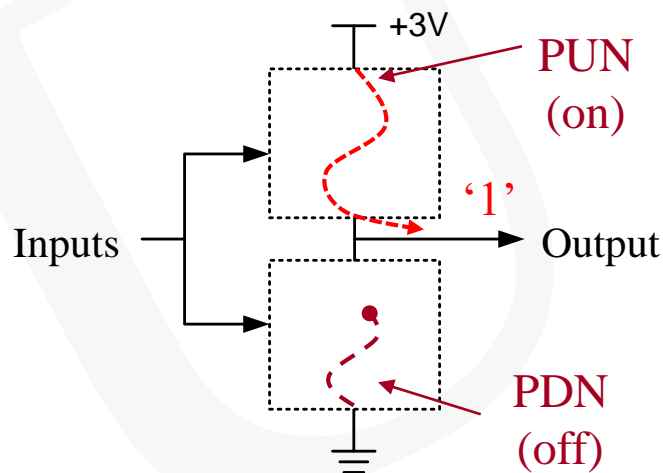- For the gate to output a '1'
 - Some path of PMOS transistors from V_{DD} to output will be on
 - We call the PMOS transistors the **Pull-Up Network (PUN)**
- For the gate to output a '0'
 - Some path of NMOS transistors from GND to output will be on
 - We call the NMOS transistors the **Pull-Down Network (PDN)**




Truth Table of a 2 input NOR gate

 

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


PDN: $G = A B \Rightarrow$ Conduction to GND


PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$

Sizing Background – Inverter

 

(a)

 


(b)

Sizing – PMOS is Slower than NMOS!

$$I_{DS-pMOS} = \frac{\mu_p C_{ox}}{2} \frac{W_p}{L} \left[2(V_{GS} - V_{T0p})V_{DS} - V_{DS}^2 \right]$$
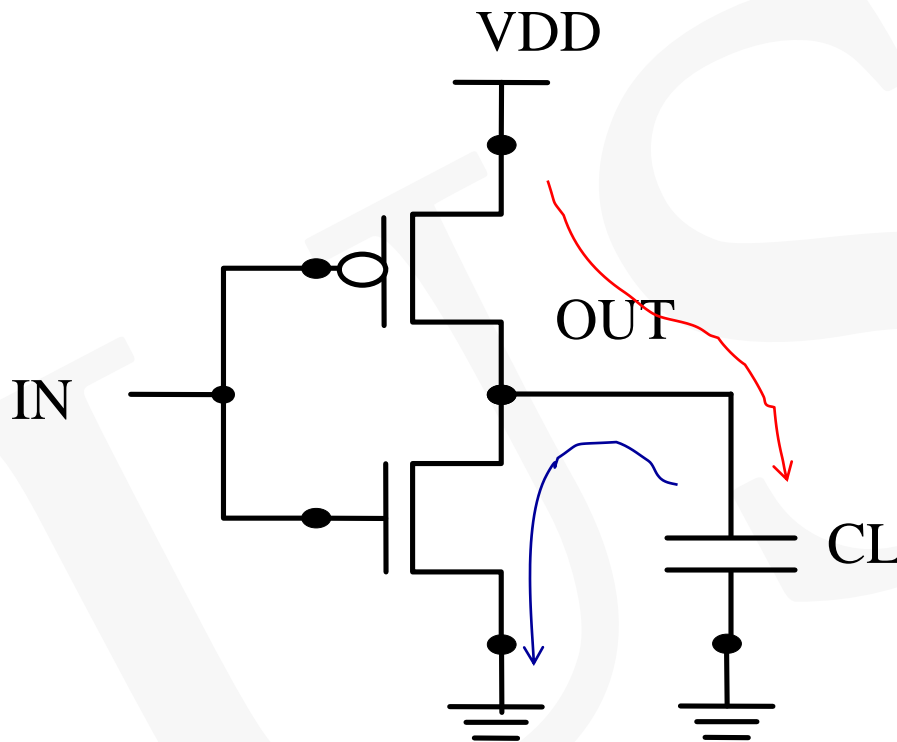
$$I_{DS-nMOS} = \frac{\mu_n C_{ox}}{2} \frac{W_n}{L} \left[2(V_{GS} - V_{T0n})V_{DS} - V_{DS}^2 \right]$$



Notes:


- $\frac{1}{R} \propto \frac{\mu W}{L}$
- $\mu_p \approx \frac{\mu_n}{2.5}$
- Sizing required to balance fall and rise time delays
- For all transistors channel is min-sized to L

Switch Delay Model


- W_p can be considered 2 to 3 times as big as W_n
- For example for inverter and assuming

$$\mu_p \approx \frac{\mu_n}{2}$$

 
$$\frac{1}{R} \propto \frac{\mu W}{L} \Rightarrow \frac{R_p}{R_n} \propto \frac{\mu_n W_n}{\mu_p W_p} = \frac{2W_n}{W_p} \Rightarrow W_p = 2W_n$$



INV

 

NAND2

 

NOR2

Input Pattern Effect on Delay


Delay is dependent on the pattern of inputs

- Low to high transition
 - both inputs go low
 - delay is $R_p/2 C_L$
 - one input goes low
 - delay is $R_p C_L$

⇒ Worst case: $R_p C_L$


- High to Low transition
 - both inputs go high
 - delay is $2R_n C_L$

$$R_p = 2R_n \rightarrow W_p = W_n$$

 


Sizing – Simple CMOS Gates

 
- Sizing of complex cells to have the same output current (hence same delay) of an inverter with a certain size:
- The ratio of the $\{W/L\}_{\text{PUN}} / \{W/L\}_{\text{PDN}}$ should be two (or higher) to make up for slow PMOS



(a)

 


(b)

 

(c)


Sizing – Complex CMOS Gates

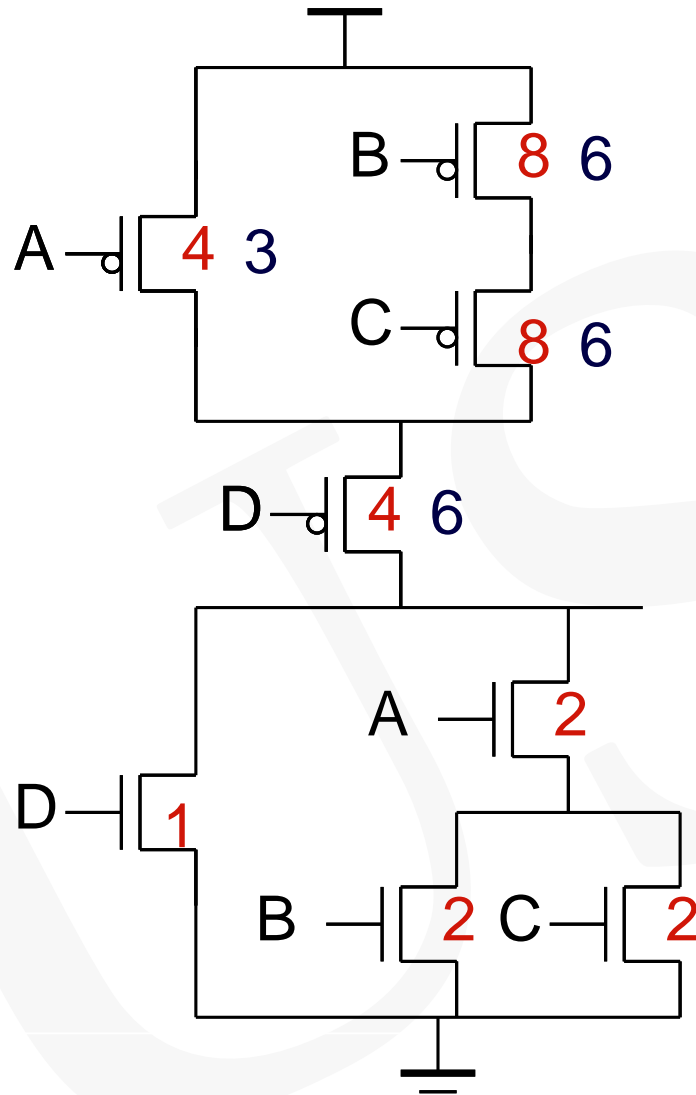


$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

Stage Sizing

 
- To drive a capacitive load **logical effort** (covered later in the course) can be used to calculate the best stage sizing for the gates in each stage
- Number of stages also important (Logic effort can be used to determine the optimal number)






XOR Design

 


(a)

 


(b)

   


(c)

 


(d)

 


(e)

 

(f)

 

(g)

 


CMOS Full-Adder Circuit

- The sum and carry_out signals of the full adder are defined as:

$$sum = A \oplus B \oplus C = ABC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

$$C_{out} = AB + AC + BC$$

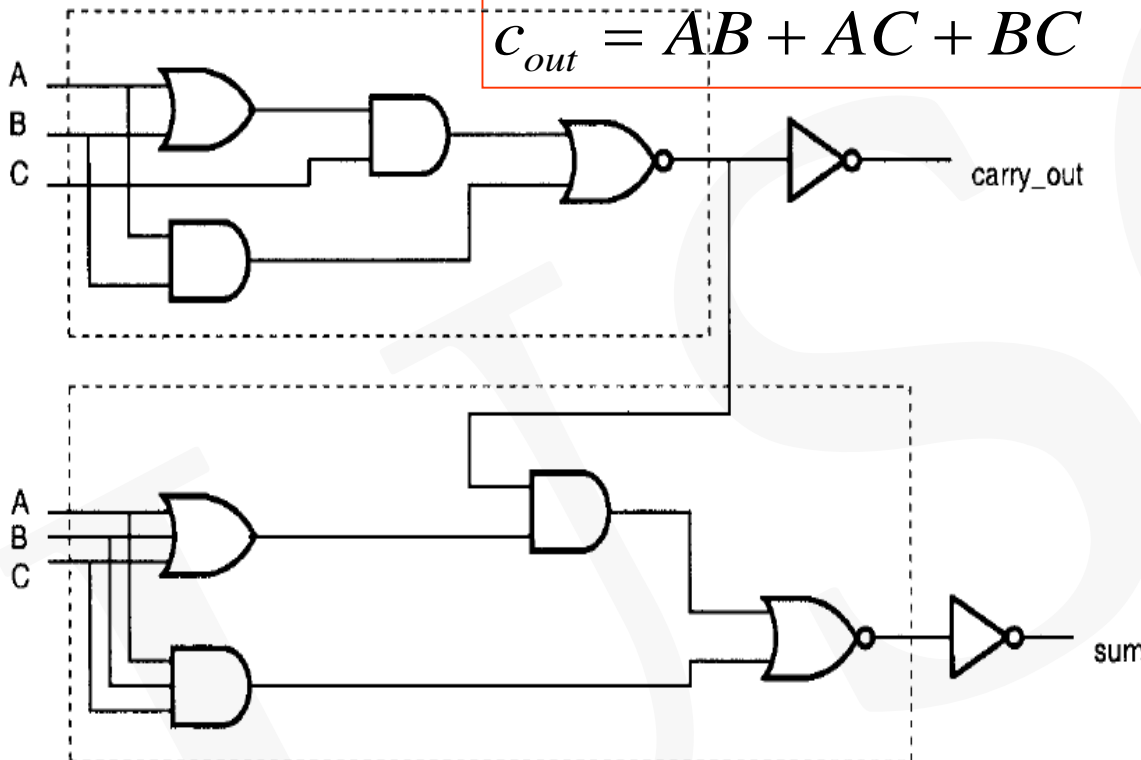

Note that we use the carry_out signal to generate the sum output:

$$sum = ABC + (A + B + C)\overline{C_{out}}$$


$$\overline{C_{out}} = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$

CMOS Full-Adder Circuit (Cont.)

$$sum = A \oplus B \oplus C = ABC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}C$$


$$C_{out} = AB + AC + BC$$

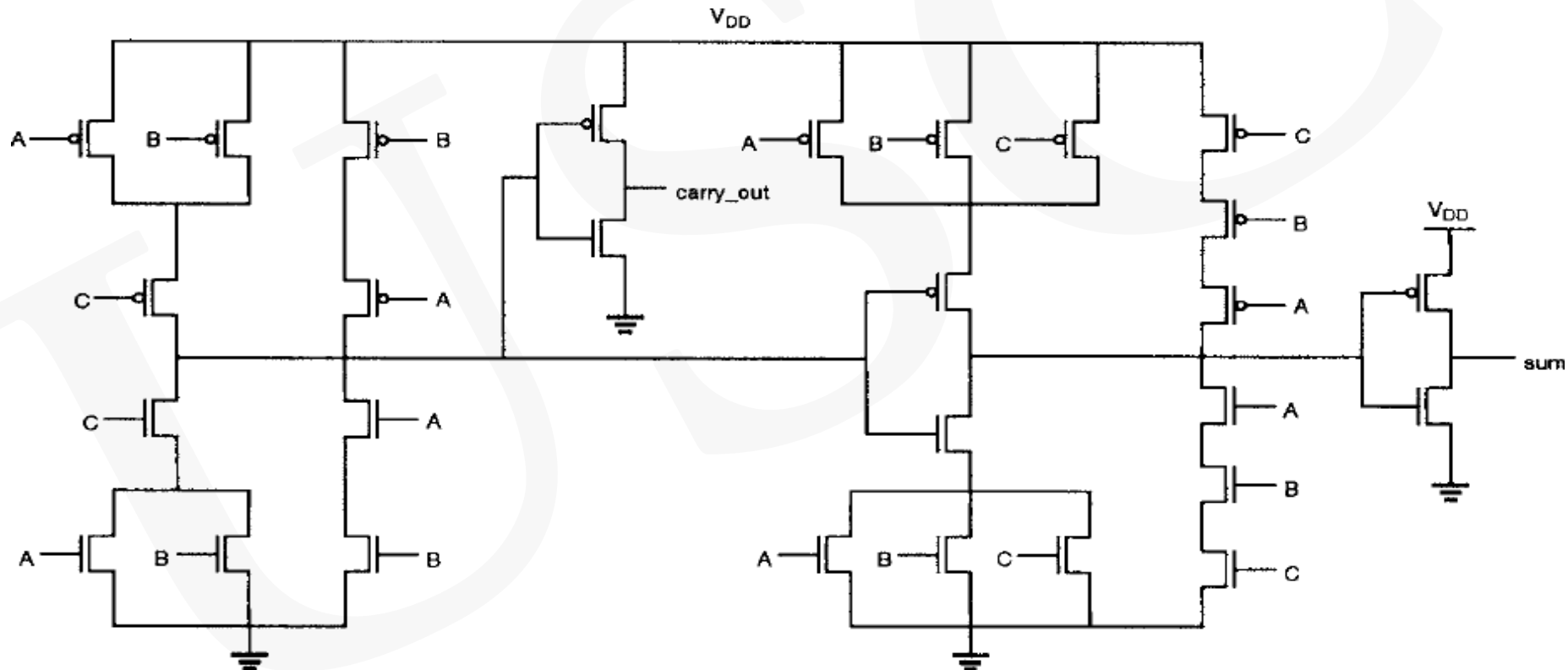- sum and carry_out circuit for a one bit full-adder:



Ripple Carry Adder (RCA)

- The simplest full-adder circuit can be constructed by a cascade-connection of full adders, where each adder stage performs a two-bit addition, produces the corresponding sum bit, and passes the carry output on to the next state
- The overall speed of RCA is limited by the delay of the carry bits rippling thru the carry chain
- The path from carry_in (C_0) to S_7 is the critical path. The second slowest path is the one from C_0 to the last carry_out (C_8)

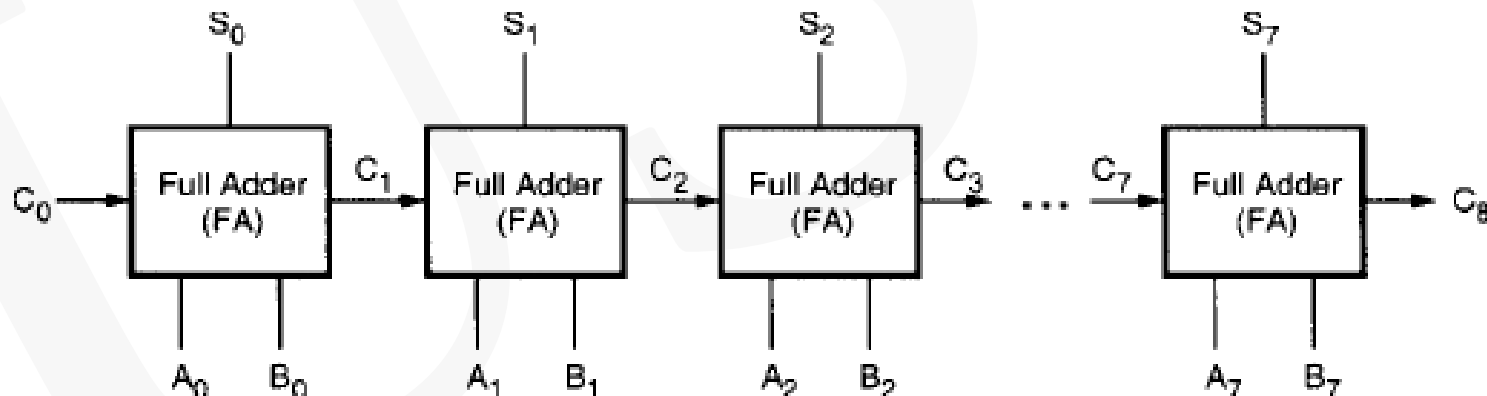


Block diagram of an 8-bit RCA chain consisting of full adders

USC

Logic Design Basics: DeMorgan's Theorem


- Inverting output of an AND gate = inverting inputs of an OR gate
- Inverting output of an OR gate = inverting inputs of an AND gate
- A function's inverse is equivalent to inverting all the inputs and changing AND to OR and vice versa

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

 

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

 

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

DeMorgan's Theorem (Cont.)

- DeMorgan is useful to write the dual of the function (useful to design PUN from PDN, because PUN is the dual of PDN)

$$F = (\overline{X} + Y) + \overline{Z} \cdot (Y + W)$$

$$\overline{F} = \overline{(\overline{X} + Y) + \overline{Z} \cdot (Y + W)}$$

$$\overline{F} = \overline{(\overline{X} + Y)} \cdot \overline{(\overline{Z} \cdot (Y + W))}$$

$$\overline{F} = (\overline{\overline{X}} \cdot \overline{Y}) \cdot (\overline{\overline{Z}} + \overline{(Y + W)})$$

$$\overline{F} = (X \cdot \overline{Y}) \cdot (Z + (\overline{Y} \cdot \overline{W}))$$